


ELECTRIC FIELD...

Capacitance


$Q = CV \rightarrow$ General formula.

$C = 4\pi\epsilon_0 R$, for an isolated metal sphere.

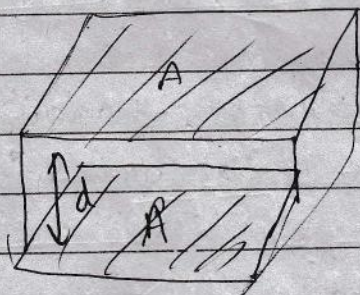Capacitance of a parallel plate capacitor



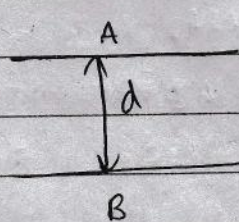An insulating medium called dielectric is put in the region between the plates such that distance between the plates is equal to thickness of dielectric.



Dielectric thickness = d

Permittivity of dielectric = ϵ

Capacitance

Area of plates in contact with dielectric = A

$C = \frac{\epsilon A}{d} \rightarrow$ capacitance bet. of this apparatus.


In a capacitor, charge in capacitor refers to charge in one of the plates of the capacitor.

This is because net charge is 0 between metal plates.

Lowest permittivity is of vacuum. Thus capacitance is ^{max.} medium when dielectric is vacuum.

Capacitors in series
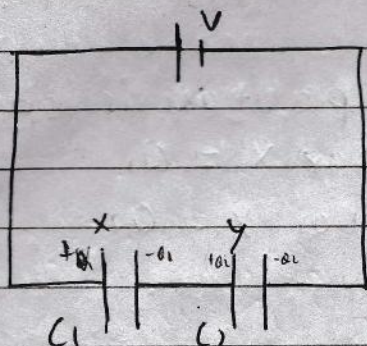
$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$



Let C be the equivalent capacitance of C_1 and C_2 in series.

$$\text{pd across } C_1 = V_1$$

$$\text{pd across } C_2 = V_2$$

$$V = V_1 + V_2$$

$$\frac{Q}{C} = \frac{Q}{C_1} = \frac{Q}{C_2} \quad [\text{By conservation of charge}]$$

$$\therefore \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$


Capacitance of a parallel plate capacitor is ~~the capacitance~~ where C is ~~the char~~ defined as $C = Q/V$, charge per unit potential difference, where Q is the charge in one of the capacitor plates and V is the pd between the plates.

Both capacitors store same charge due to conservation of charge/current when in series.

While a number of capacitor are connected in series, effective capacitance is smaller than the individual smallest capacitance.

Capacitors in parallel

$$C = C_1 + C_2$$

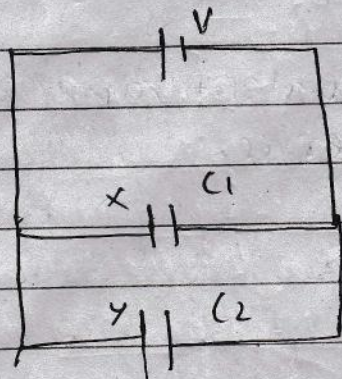

Pd across both capacitors is same.

Charge in capacitor X = Q_1


Charge in capacitor Y = Q_2

$$Q = Q_1 + Q_2$$


$$C \cdot V = C_1 V + C_2 V$$

$$\therefore C = C_1 + C_2$$

#

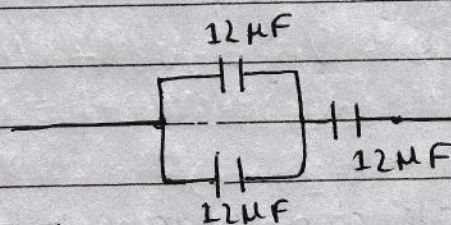


$$C = 8 \mu F$$

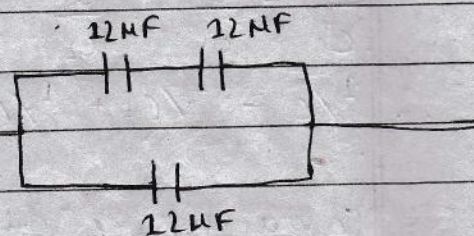

$$C = 18 \mu F$$

#

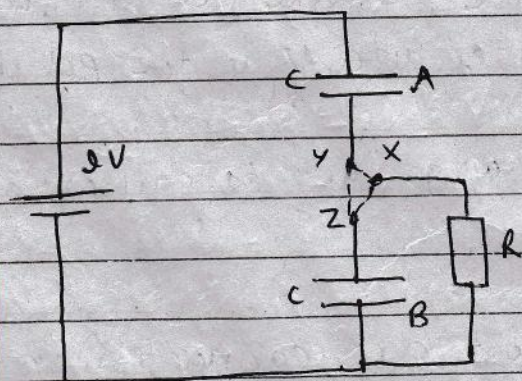


When X and Y are connected, pd across A is 3V

When Y and Z are connected, pd across A is 4.5V. - Case I

Immediately after Case I if YZ is disconnected and XZ is connected

capacitor discharges and pd across R is 4.5V.

Energy stored in a charged capacitor

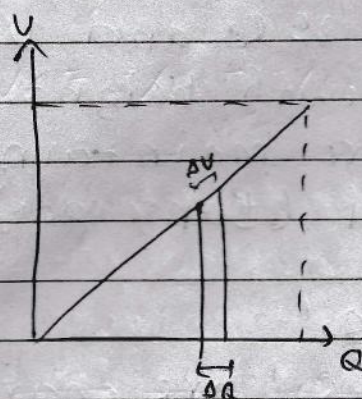

$$Q = CV$$

$$V = \frac{1}{C} Q$$

Charge in capacitor plate (initial) = 0

Initial pd between plates of capacitor = 0
When we go on adding charge to the capacitor, the pd between two plates also goes on increasing linearly.

Work done in delivering a charge Q to the capacitor plate

= charge \times pd

$$= Q \times \frac{1}{2} (V_{avg})$$

$$= \frac{1}{2} QV$$

Final charge in capacitor = Q


Final pd between the plates = V

The final charge (Q) is transferred to the plate of the capacitor at an average pd. of $\frac{0+V}{2}$, i.e. the capacitor is charged at an avg. potential of $\frac{V}{2}$.

$$\therefore U = \frac{1}{2} QV, \frac{1}{2} CV^2, \frac{1}{2} \frac{Q^2}{C}$$


$\frac{1}{1000 \text{ nF}}$ 50V
 $Q = 0.05 \text{ C}$

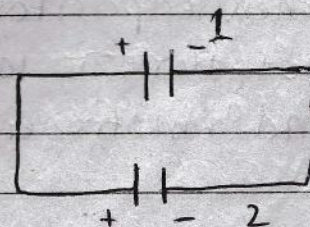$\frac{2}{2000 \text{ nF}}$ 25V
 $Q = 0.05 \text{ C}$




Describe the flow in the circuit

$$P(t) =$$

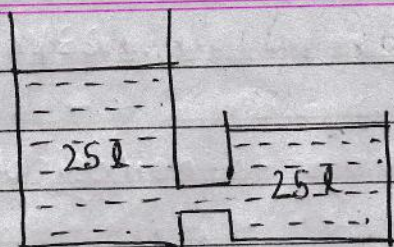

capacitor 1 capacitor 2 water level (same pd)

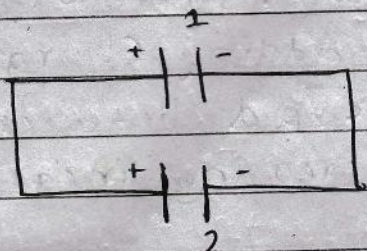The case resembles this case where $Q = 25 \mu\text{C}$ and V is analogous with height, i.e. the capacitors maintain same



$Q_1 + Q_2 = Q_1' + Q_2'$
where Q_1' and Q_2' are charges in capacitors 1 and 2 after sharing charges.

$$C_1 V_1 + C_2 V_2 = (C_1 + C_2) V \quad [\text{pd will be same}]$$

$$\therefore V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

$$C_1 + C_2$$

$$\therefore Q_1' = C_1 V = 0.033 \text{ C}$$

$$\therefore Q_2' = C_2 V = 0.066 \text{ C} \quad 0.067 \text{ C}$$

$$\therefore V = \frac{0.05 + 0.05}{3000 \times 10^{-9} \text{ F}}$$

$$\therefore V = 33.3 \text{ V} \quad (100/3) \quad \therefore \text{More charge is with more capacitance}$$

$$\text{Energy before} = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 = 1.25 + 0.625 = 1.875 \text{ J}$$

$$\text{Energy after} = \frac{1}{2} (C_1 + C_2) V^2 = 1.667 \text{ J}$$

When capacitors share charge, charge is conserved but there is loss of energy due to thermal heating and kinetic energy of charges.

Charging and discharging of a capacitor through resistor

Time constant of a RC circuit.

$$\tau = RC$$

Time that it takes for a capacitor to discharge upto 36.8% of its original charge stored.

$$Q = CV, V = Q/C$$

Current through Resistor R is $I = -dQ/dt$ and $V = IR$

$$a) \frac{Q}{C} = -\frac{dQ}{dt} \times R$$

$$b) \int_{Q_0}^Q \frac{dQ}{Q} = \int_0^t \frac{-dt}{CR} \quad \text{where } Q_0 = \text{initial charge at time 0, } Q = \text{final charge @ time } t$$

$$c) [\ln Q]_{Q_0}^Q = -\frac{1}{CR} [t]_0^t$$

$$d) \ln Q - \ln Q_0 = -t/CR$$

$$e) \ln (Q/Q_0) = -t/CR$$

$$f) Q/Q_0 = e^{-t/CR}$$

$$g) \therefore Q = Q_0 \cdot e^{-t/CR}, V = V_0 e^{-t/CR}, I = I_0 e^{-t/CR}$$

$$Q = Q_0 \cdot e^{-t/CR}$$

If $t = CR$ --- finding time constant.

$$\Rightarrow Q = Q_0 e^{-1}$$

$$\Rightarrow Q = \frac{1}{e} Q_0$$

$$\therefore Q = 0.368 Q_0$$

36.8% of original charge.